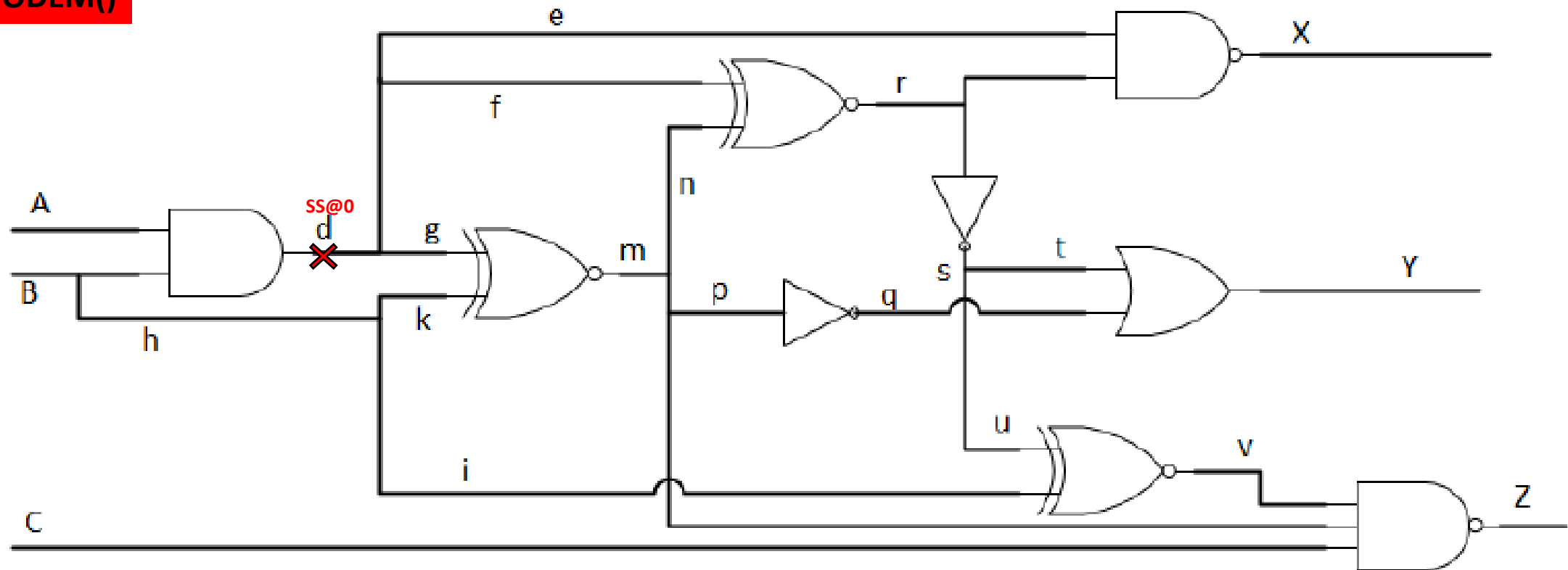


PODEM

d – SS@0


EE658 – Diagnosis and Design of Reliable Digital Systems
 Professor Tabar
 Fei Wu

PODEM()



All initial values are considered X, including the faulty node.


Objective()

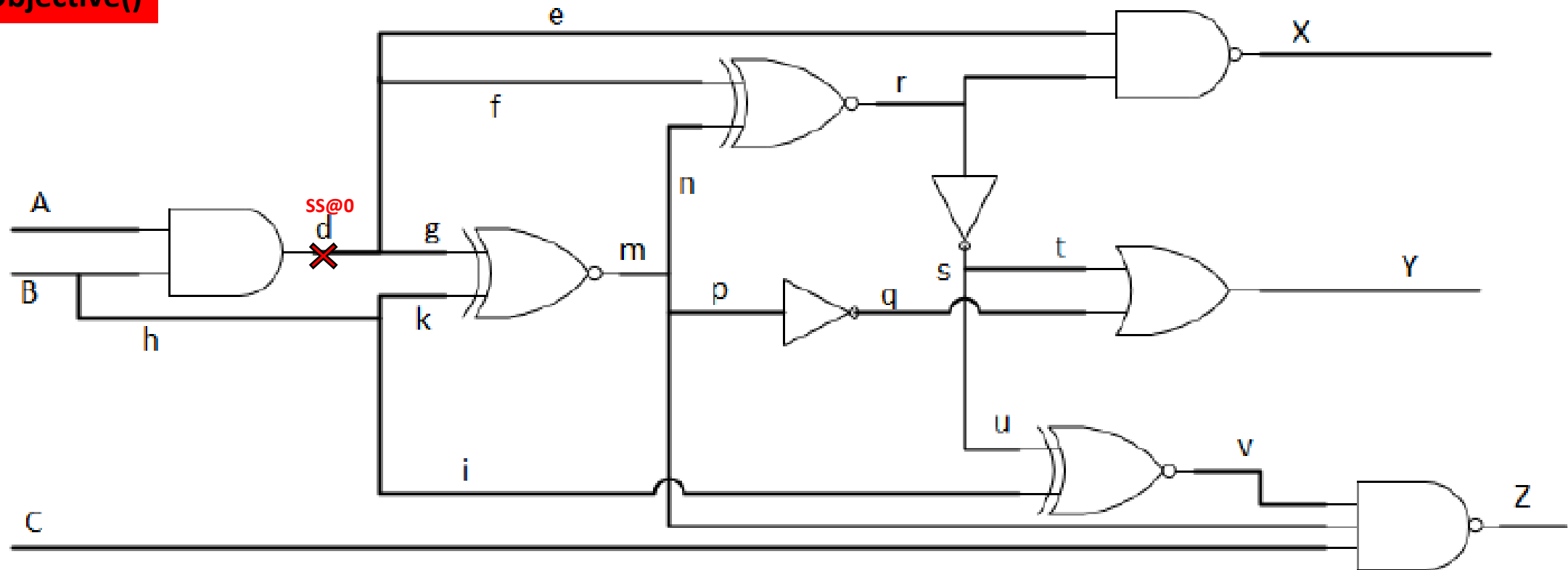


Fault: AND_d SS@0, current value of AND_d = X

Objective: {AND_d, 1}


Backtrace(AND_d, 1)

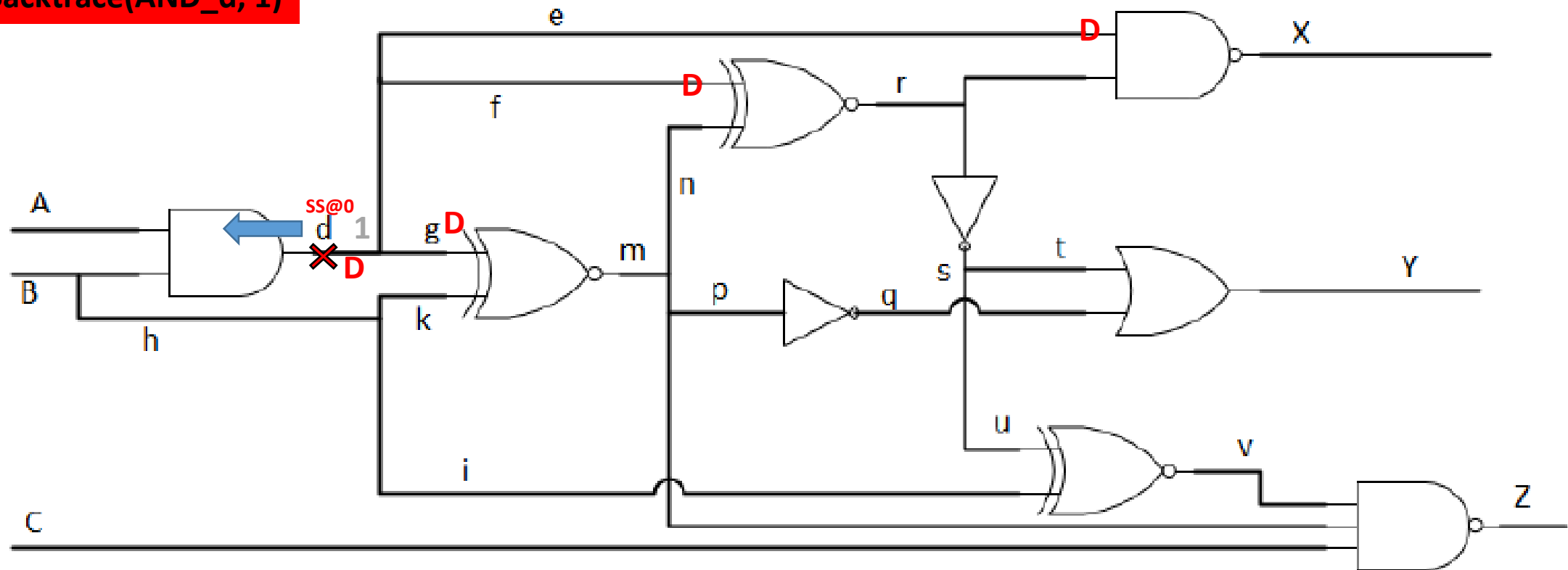

Backtrace(AND_d, 1)

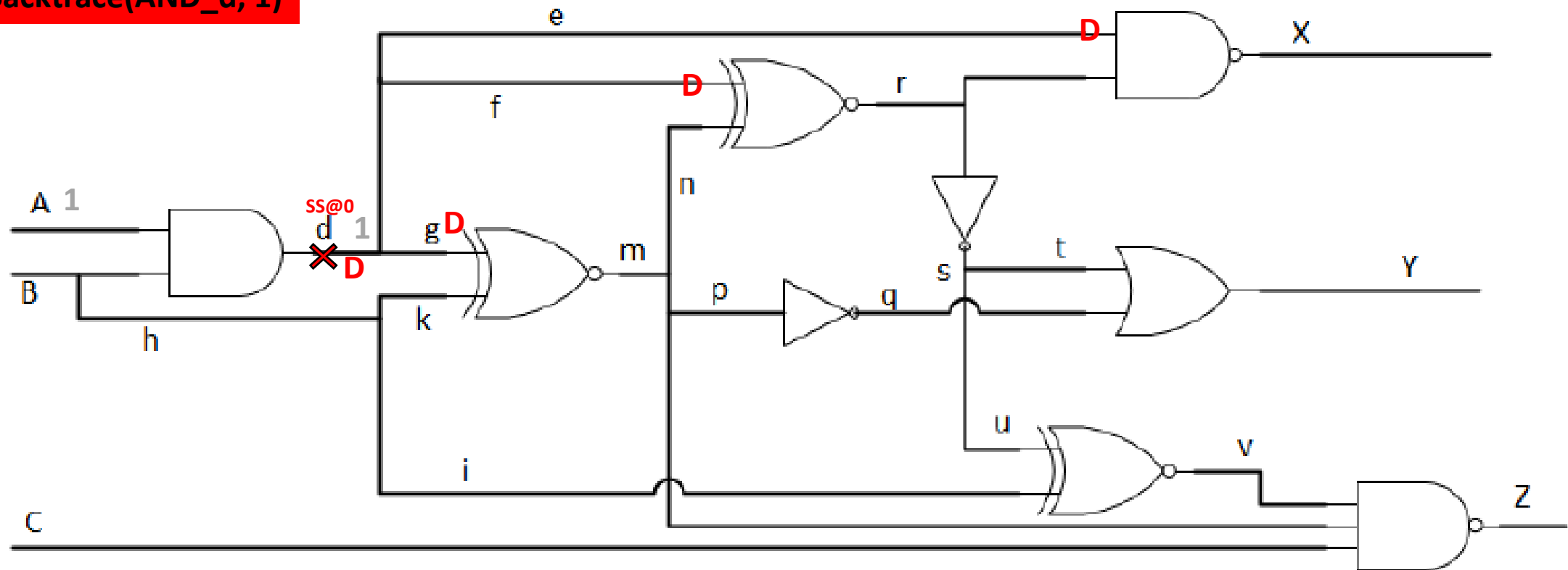


Backtrace(AND_d, 1)

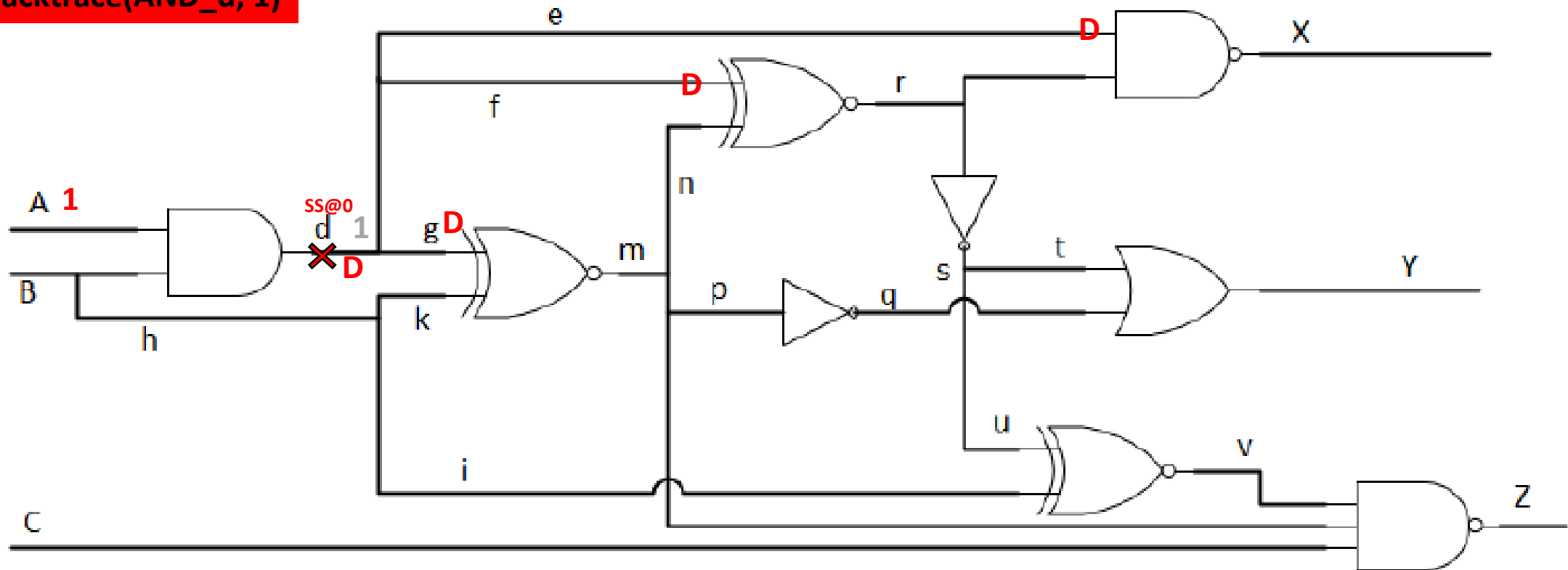


Note: PI can be considered as a gate in the algorithm.

A is PI, return (PI_A, 1)

ImPLY(PI_A,1)

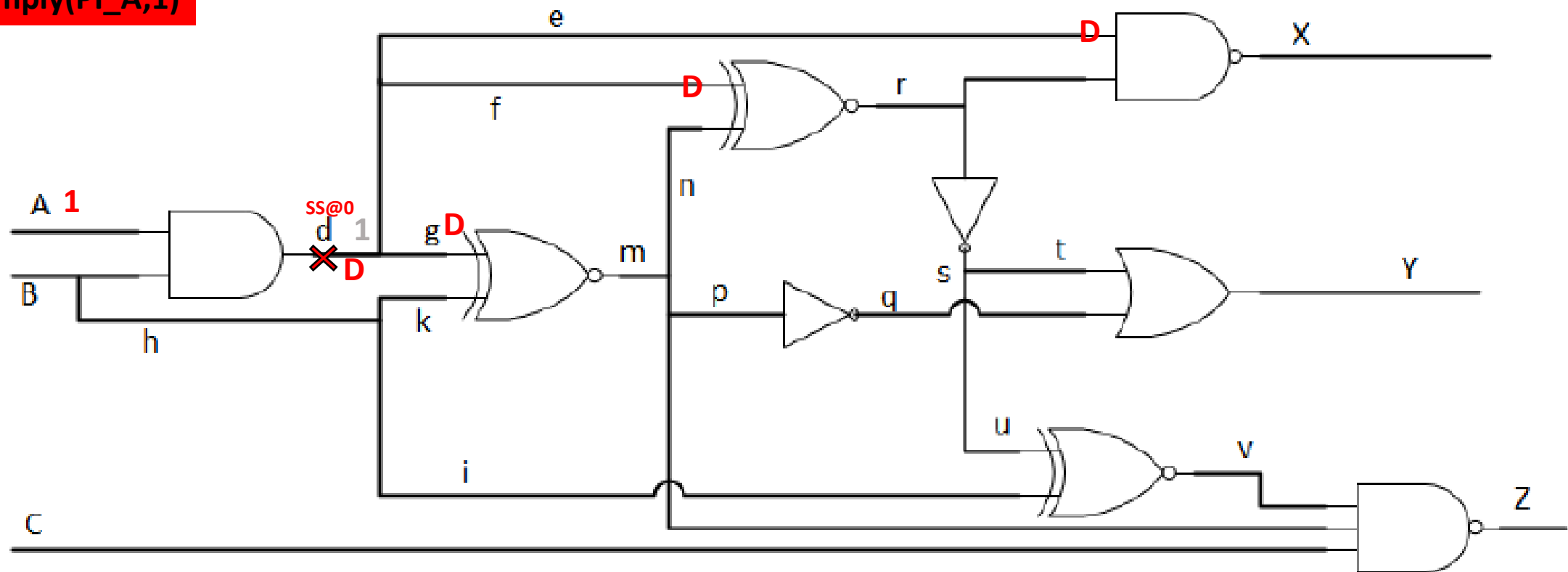


PODEM

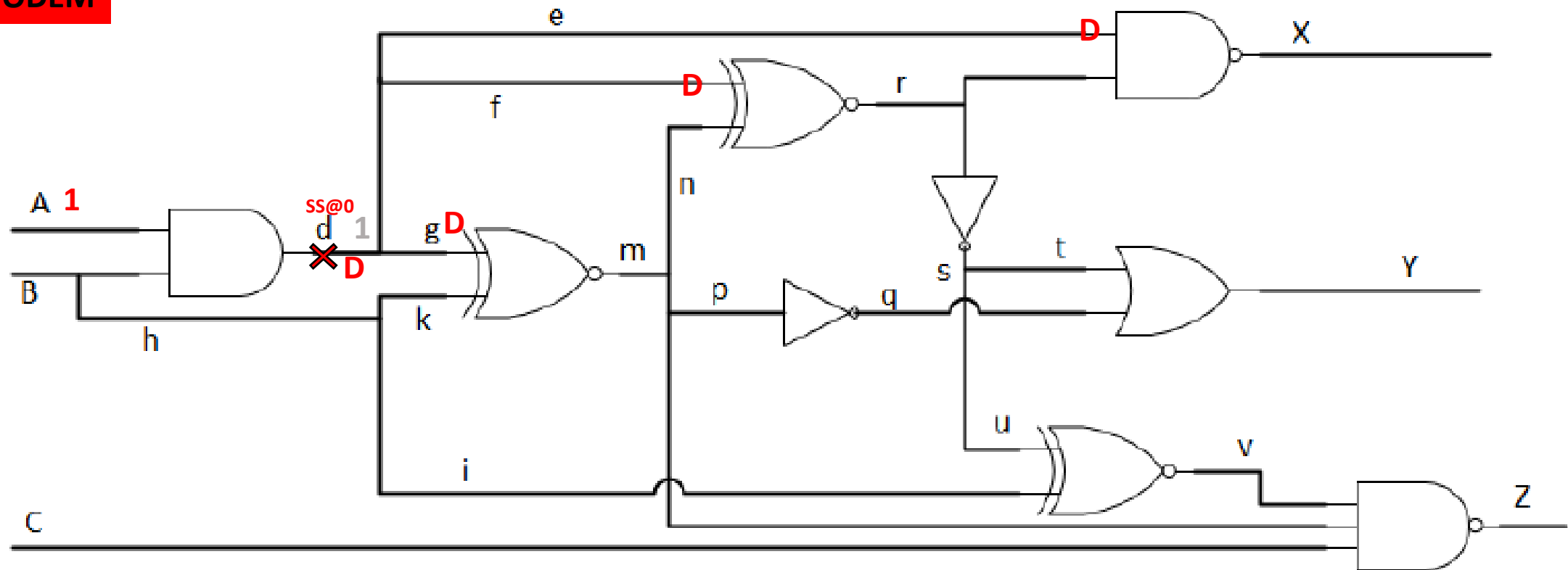

Error is not at the output
Test is possible(no conflicts)

Objective

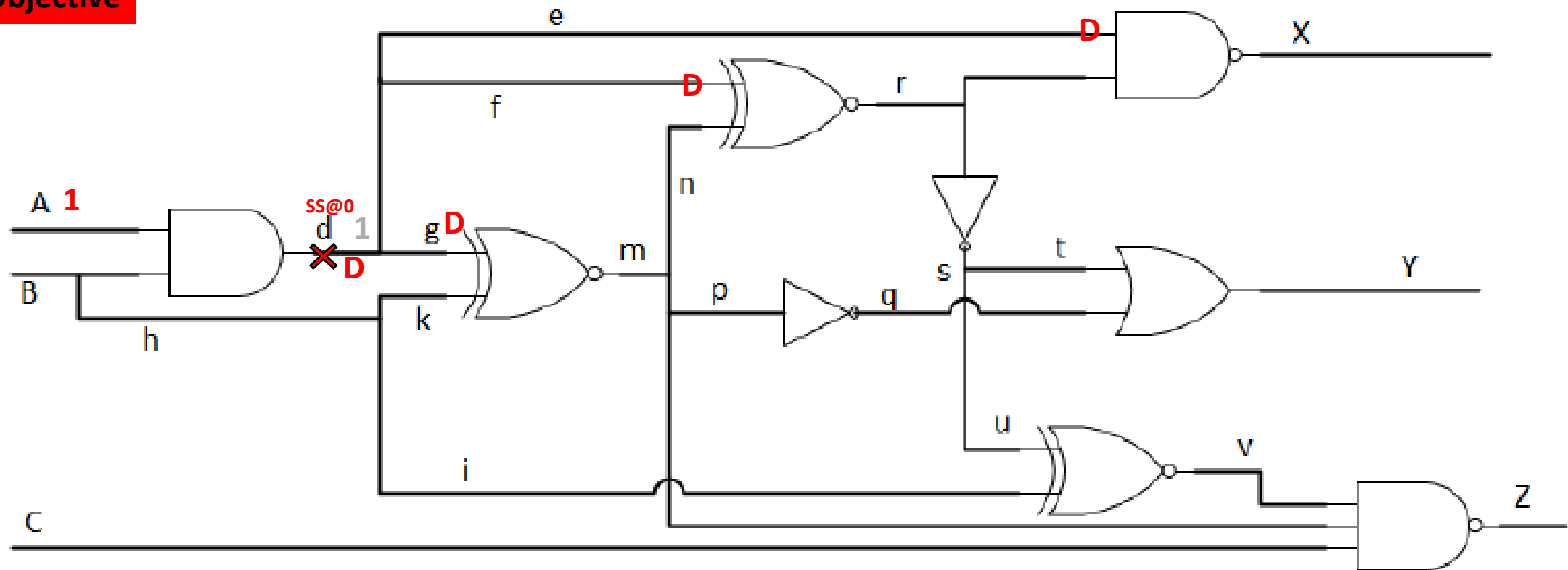


Error is not at the output

Test is possible(no conflicts)

D-frontier={NXOR_m,NAND_X, NXOR_r}

Objective={NXOR_m,1}

Backtrace(AND_d, 1)

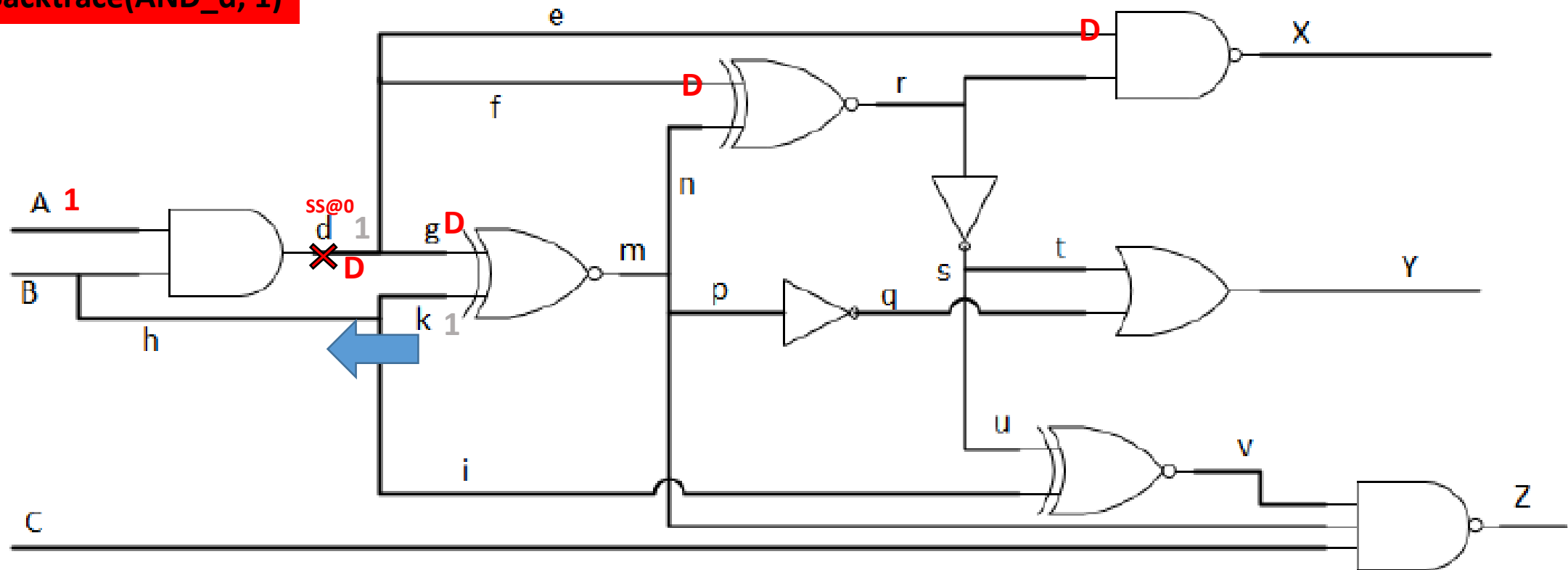


Error is not at the output

Test is possible(no conflicts)


D-frontier={NXOR_m,NAND_X, NXOR_r}

Objective={NXOR_m,1}


Backtrace(AND_d, 1)

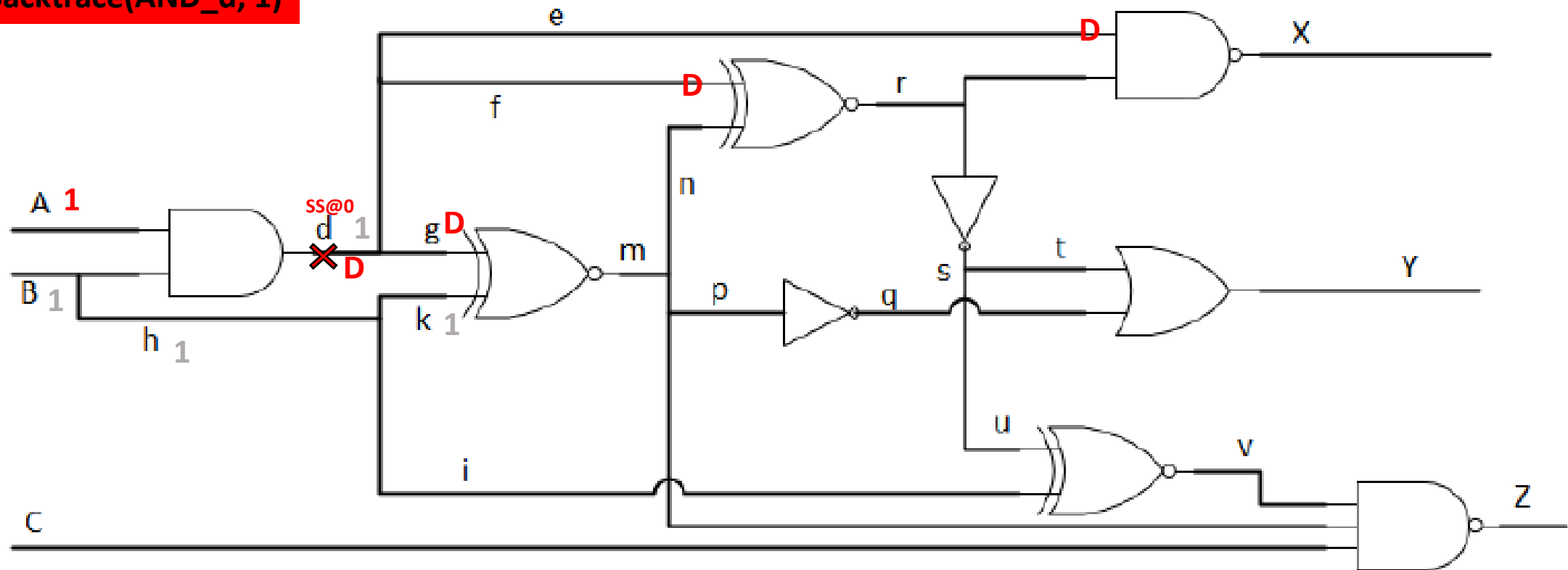

Imply(PI_B, 1)

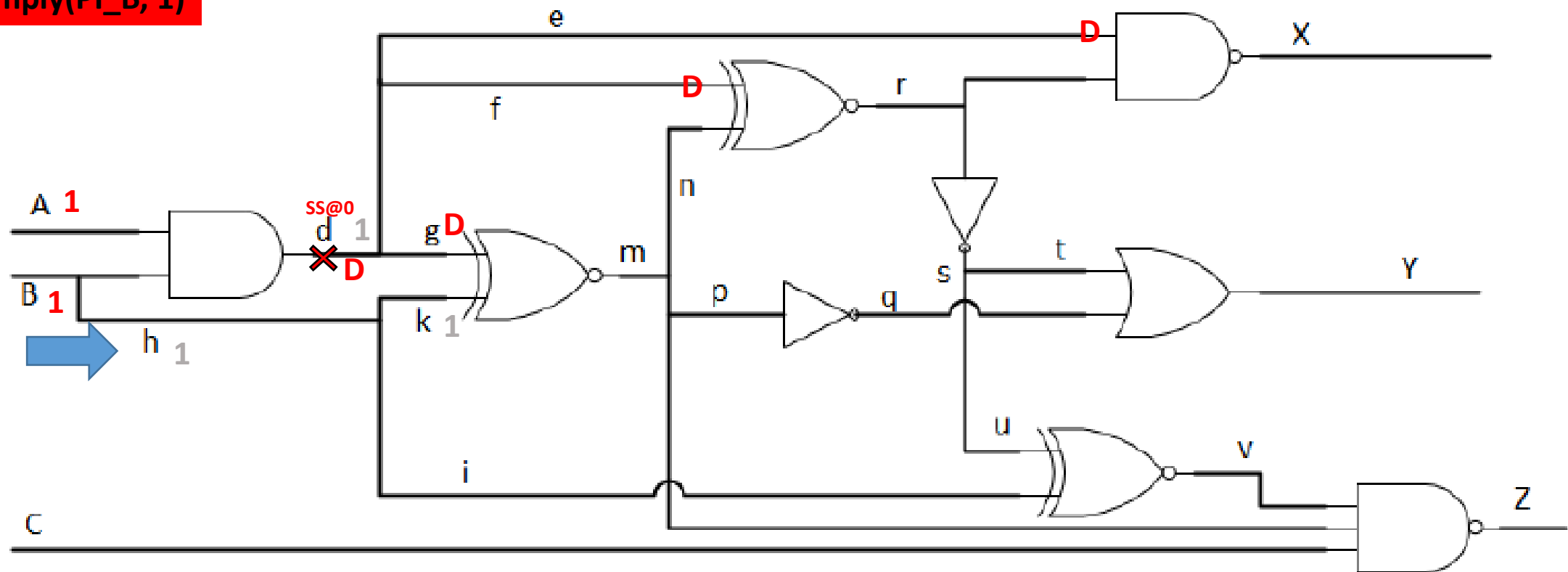

ImPLY(PI_B, 1)

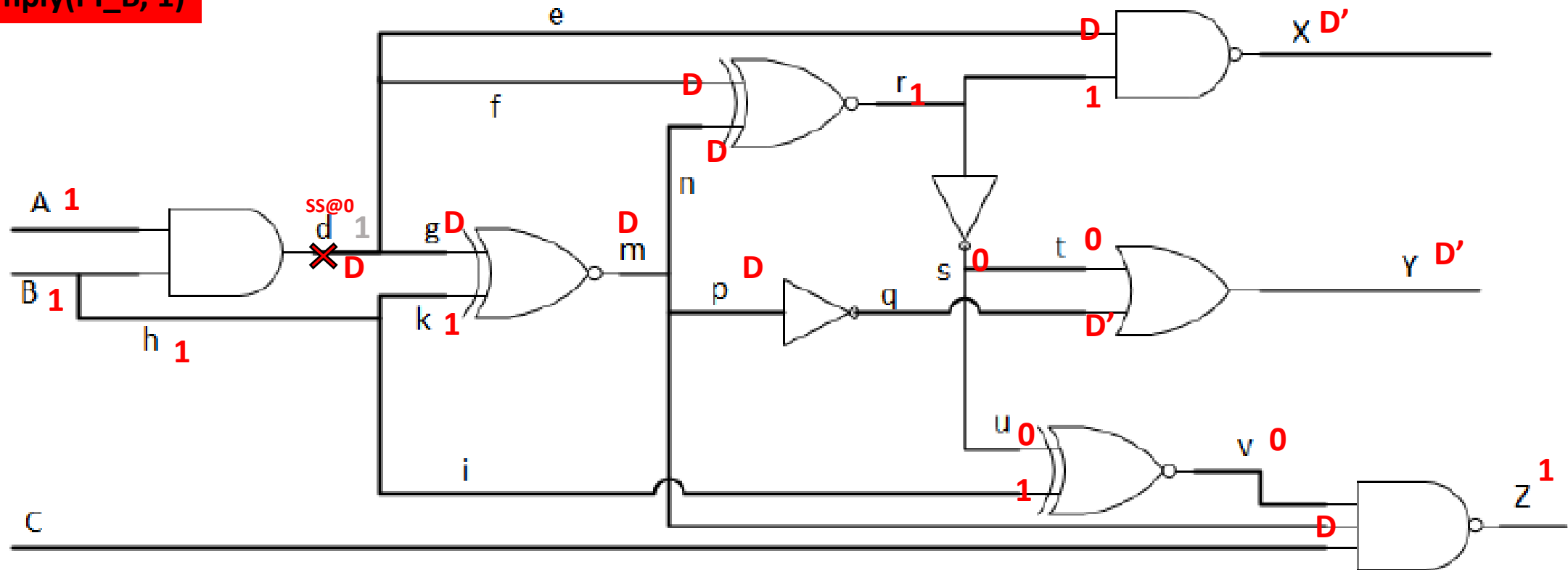

Note: error is at the output

SUCCESS

$$T = \{1, 1, X\}$$